 


Gates



SOPs and POSs

We can create boolean algebra expressions for truth tables.

**Minterm:** Corresponds to each row of truth table, i.e.  $m_3 = \overline{x_2}x_1x_0$  such that when  $3 = 0b011$  is substituted in,  $m_3 = 1$  and  $m_3 = 0$  otherwise.

**Maxterm:** They give  $M_i = 0$  if and only if the input is  $i$ . For example,  $M_3 = x_2 + \overline{x_1} + \overline{x_0}$ .

**SOP and POS:** Truth tables can be represented as a sum of minterms, or product of maxterms.

- Use minterms when you have to use **NAND** gates and maxterms when you have to use **NOR** gates.
- When converting expressions to its dual, it's often helpful to negate expressions twice, or draw out the logic circuit.

Cost


The cost of a logic circuit is given by

cost = gates + inputs (1)

If an inversion (NOT) is performed on the primary inputs, then it is not included. If it is needed inside the circuit, then the NOT gate is included in the cost.

Karnaugh Map

 Method of finding a minimum cost expression: We can map out truth table on a grid for easier pattern recognition. Example of a four variable map is shown below:



and the representation is  $\overline{x_2} \cdot \overline{x_4} + x_2 \cdot x_1 + \overline{x_4} \cdot x_2$  when using *minterms*. To use *maxterms*, we take the intersection of sets that don't include blocks of 0s. For example,  $(\overline{x_2} \cdot \overline{x_1})(\overline{x_2} + x_1 + x_4)$ . Some rules:

- Side lengths should be powers of 2 and be as large as possible.
- Use **graycoding**: adjacent rows/columns should share one bit.

Minimization Procedure


1. Generate all prime implicants for given function  $f$
2. Find the set of essential prime implicants
3. Determine the nonessential prime implicants that should be added.

Common Logic Gates

- **Mux 2→1:**  $\text{mux2to1}(s, x_0, x_1) = \overline{s}x_0 + sx_1$
- **Not:**  $\text{not}(x) = \text{nand}(x, x) = \text{nor}(x, x)$
- XOR acts as modular arithmetic.
- Multiplexers are functionally complete.  $\text{AND} = \text{mux}(x, y, 1)$ ,  $\text{OR} = \text{mux}(x, 0, y)$ .

RS Latch + Gated D Latch

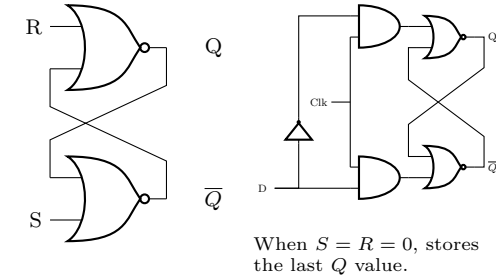
Sequential circuits depend on sequence of inputs. A **SR Latch** are cross-coupled NOR gates.



D Flip Flops

Consists of two gated D latches, connected in series and both connected to the same clock. However, clock input for the first D latch is inverted. When the clock rises up,  $Q$  stores value of  $D$ .

T Flip Flops

 

SystemVerilog Logic Operators

bitwise AND	&	bitwise OR	
bitwise NAND	~&	bitwise NOR	~
bitwise XOR	^	bitwise XNOR	^^
logical negation	!	bitwise negation	~
concatenation	{}	replication	{ { }}

- **blocking assignment** =: executed in the order they are specified.
- **Nonblock assignments** <= executed in parallel.
- Use logic instead of reg/wire (4-state type)
- Use **always\_comb** for combinational, **always\_ff** for sequential logic

Case Statements

```
module mux(  
    input logic [2:0] MuxSelect,  
    input logic [4:0] Input,  
    output logic Out  
);  
    always_comb begin  
        case (MuxSelect)  
            3'b000: Out = Input[0];  
            // ...  
            3'b100: Out = Input[4];  
            default: Out = 1'bx;  
        endcase  
    end  
endmodule
```

Half Adder

```
module HA(  
    input logic x, y,  
    output logic s, c  
);  
    assign s = x ^ y;  
    assign c = x & y;  
endmodule
```

Full Adder

```
module FA(  
    input logic a, b, c_in,  
    output logic s_out, c_out  
);  
    logic w1, w2, w3;
```

```
HA u0(.x(a), .y(b), .s(w1), .c(w2));  
HA u1(.x(c_in), .y(w1), .s(s_out), .c(w3));  
assign c_out = w2 | w3;  
endmodule
```

D Flip Flop

```
module D_ff(  
    input logic D, clk,  
    output logic Q  
);  
    always_ff @(posedge clk)  
        Q <= D;  
endmodule
```

T Flip Flops

```
module t_ff(  
    input logic Clock, Clear_b, T,  
    output logic Q  
);  
    always_ff @(posedge Clock, negedge Clear_b)  
        if (Clear_b == 1'b0)  
            Q <= 1'b0;  
        else  
            Q <= T ^ Q;  
    end  
endmodule
```

Registers

```
module reg8(  
    input logic clk,  
    input logic [7:0] D,  
    output logic [7:0] Q  
);  
    always_ff @(posedge clk)  
        Q <= D;  
endmodule
```

ModelSim Do Files

```
# set working dir, where compiled verilog goes  
vlib work  
# compile all modules in mux.v to working  
# dir could also have multiple verilog files  
vlog mux.v  
#load simulation using mux as the  
# top level simulation module  
vsim mux  
#log sgnls and add sgnls to waveform window  
log { /* }  
# add wave { /* } would add all items in  
# top level simulation module  
add wave { /* }  
# set input values using the force command  
# signal names need to be in { } brackets  
force {SW[0]} 0  
force {SW[1]} 0  
run 10ns
```

ModelSim and Other Lab Things

- **FGPA:** Field Programmable Gate Array
- To repeat signals, use this syntax:  
  
force {MuxSelect[2]} 0 0ns,  
1 {4ns} -r 8ns  
  
which starts at 0 at 0ns, 1 at 4ns, and repeats every 8 ns.
- On the DE1-SoC board, hex thing is red if 0 and white if 1.

Frequency Dividers

- To half the frequency, connect  $\overline{Q}$  to  $D$  on the same gated D latch.
- To quarter the frequency, connect  $\overline{Q}$  to the clock of the next gated D latch (which is set up the same as the half frequency case).
- To reduce frequency by  $2k$ , connect  $k$  D latches connected in series ( $D$  to  $Q$ ) and to the same clock. First  $D$  is connected to last  $Q$ . The last  $Q$  will have a reduced frequency of  $2k$ .

Resets

- Active High/Low: Resets when Signal is 1/0
- Synchronous High/Low: Resets during positive/negative edge

Finite State Machines

Steps

1. State Diagram

Table
2. State Table

5. Synthesize Circuit
3. State Assignment
4. State-Assigned

6. Celebrate!

Step 2: State Table Example

Present State	Next State	Output (z)
A	A B	0
B	A C	0
⋮	⋮ ⋮	⋮
G	A C	1

Step 3: State Assignment Example

- Using **one-hot encoding**: Choose number of flip flops: 7 (since 7 states)
- Choose state codes:
  - A = 0000001, B=0000010, ..., G=1000000

Alternatively use 3 flip flops to represent state codes as 000, 001, 010, etc.

Step 4: State-Assigned Table Example

By convention, use *y* for input and *Y* for output.

<i>y</i> <sub>3</sub> <i>y</i> <sub>2</sub> <i>y</i> <sub>1</sub>	<i>Y</i> <sub>3</sub> <i>Y</i> <sub>2</sub> <i>Y</i> <sub>1</sub> ( <i>W</i> = 0)	<i>Y</i> <sub>3</sub> <i>Y</i> <sub>2</sub> <i>Y</i> <sub>1</sub> ( <i>W</i> = 1)	<i>z</i>
000	000	001	0
001	000	010	0
⋮	⋮	⋮	⋮
110	000	010	1

Step 5: Synthesize Example

We first write boolean algebra expressions for the outputs  $Y_n = f_n(y_1, y_2, y_3, W)$  and  $z = g(y_1, y_2, y_3)$ . For each flip flop *i*, the input is *Y<sub>i</sub>* and the output is *y<sub>i</sub>*. The output then branches off into two paths:

- The first path goes into the function *g*(*y<sub>1</sub>*, *y<sub>2</sub>*, *y<sub>3</sub>*) and leads to output *z*
- The second path goes into the function *f<sub>n</sub>m*(*y<sub>1</sub>*, *y<sub>2</sub>*, *y<sub>3</sub>*, *W*) and **loops back** to *Y<sub>n</sub>*.

The D flip flops are connected to same clock and reset signal.

Execution in SystemVerilog

```
module FSM(
    input logic Clock, Resetn, w,
    output logic z,
    output logic [3:0] CurState
);
    logic [3:0] y_Q, Y_D;
    typedef enum logic [3:0] {
        A = 4'b0000,
        B = 4'b0001,
        // ...
        G = 4'b0110
    } state_t;
    always_comb begin
        case (y_Q)
            A: Y_D = w ? B : A;
            // ...
            G: Y_D = w ? C : A;
            default: Y_D = A;
        endcase
    end
    always_ff @(posedge Clock) begin
        if (!Resetn)
```

```
            y_Q <= A;
        else
            y_Q <= Y_D;
    end
    assign z = (y_Q == F) | (y_Q == G);
    assign CurState = y_Q;
endmodule
```

RISC-V Assembly

Registers

- x0 (zero): Hardwired zero, x1 (ra): Return address, x2 (sp): Stack pointer
- x5-x7, x28-x31 (t0-t6): Temporary (caller-saved)
- x8-x9, x18-x27 (s0-s11): Saved (callee-saved)
- x10-x17 (a0-a7): Function args/return values
- x3 (gp): Global pointer, x4 (tp): Thread pointer

Instructions

Let a0=1, a1=2, a2=0b1010.

Instruction	Example	Result
ADDI	addi a3, zero, 3	a3 = 3
ADD	add a3, a0, a0	a3 = 1 + 1
SUB	sub a3, a0, a0	a3 = 1 - 1
MUL	mul a3, a0, a0	a3 = 1 * 1
SLLI	slli a3, a2, 1	a3 = 0b10100
SRLI	srl_i a3, a2, 1	a3 = 0b0101
SRAI	srai a3, a2, 1	a3 = 0b1101
AND	and a3, a1, a0	a3 = (1 and 2) = 0

Memory Stuff

- JAL: Jump and Link - stores return address in ra (x1)
- JALR: Jump and Link Register - indirect jump
- Stacks: Manual push/pop:
  - addi sp, sp, -8 then sw a0, 0(sp)
- Each instruction is 4 bytes (32-bit) in RV32.

Load and Store

- lw a0, offset(a1): Load word;
- sw a0, offset(a1): Store word
- la a0, label: Load address (pseudo-instruction)
- lb/lbu - load byte (signed/unsigned), lh/lhu - load halfword
- sb - store byte, sh - store halfword

Conditionals

RISC-V has no flags. Branch instructions: beq (equal), bne (not equal), blt/bge (less/greater signed), bltu/bgeu (unsigned). Set: slt, slti, sltu, sltiu.

Interrupts

1. Set mtvec CSR (trap vector)
2. Enable interrupts in mstatus (MIE bit)
3. Enable sources in mie CSR
4. Configure PLIC/CLIC
5. Save context on trap entry
6. Read mcause CSR for cause
7. Handle in ISR, clear PLIC pending bit
8. Restore context, return with mret

RISC-V Assembly Example Code

Enabling Interrupts

```
li sp, 0x10000 # Initialize stack
la t0, trap_handler
csrw mtvec, t0 # Set trap vector
li t0, 0x8
csrs mstatus, t0 # Enable interrupts (MIE)
li t0, 0x800
csrs mie, t0 # Enable external int (MEIE)
li t0, 0xFF20058
li t1, 0b1001
sw t1, 0(t0) # Enable key3, key0
```

Check Cause of Interrupt

```
trap_handler:
    addi sp, sp, -32
    sw t0, 0(sp); sw t1, 4(sp); sw a0, 8(sp)
    sw a1, 12(sp); sw ra, 16(sp)
    csrr t0, mcause # Read cause
    li t1, 0x8000000B
    bne t0, t1, error_trap
    jal ra, key_isr
    j exit_trap
error_trap:
    j error_trap
exit_trap:
    lw t0, 0(sp); lw t1, 4(sp); lw a0, 8(sp)
    lw a1, 12(sp); lw ra, 16(sp)
    addi sp, sp, 32
    mret
```

ISR Subroutine

```
key_isr:
    addi sp, sp, -20
    sw t2, 0(sp); sw t3, 4(sp)
    sw t4, 8(sp); sw t5, 12(sp)
    la t5, CURR_VALUE
    lw t4, 0(t5)
    li t2, 0xFC20005C
    lw t3, 0(t2)
    li t0, 0b1000
    bne t3, t0, key0
    beq t4, zero, endisr
    addi t4, t4, -1
    sw t4, 0(t5)
    j endisr
key0:
    # code for key 0
endisr:
    lw t2, 0(sp); lw t3, 4(sp)
    lw t4, 8(sp); lw t5, 12(sp)
    addi sp, sp, 20
    ret
```

Polled IO with Timer

```
.text
.globl _start
_start:
    li a0, 0xFFFFEC600
    li a1, 2000000000
    sw a1, 0(a0)
    li a1, 0b111
    sw a1, 8(a0)
    li s0, 0; li s1, 0; li s2, 0 # sec,min,hr
poll:
    lw a1, 12(a0)
    beq a1, zero, poll
    sw a1, 12(a0)
    addi s0, s0, 1
    li t0, 60
    bne s0, t0, poll
    li s0, 0
    addi s1, s1, 1
    bne s1, t0, poll
    li s1, 0
    addi s2, s2, 1
    li t0, 24
    bne s2, t0, poll
    li s2, 0
    j poll
```

Exception Vector Table

```
.align 2
trap_vector:
    j trap_handler # Direct: all to one handler
# Vectored: mtvec.MODE=1, base + 4*cause
# 0x00:Exception 0x04:Supervisor SW int
# 0x0C:Machine SW int 0x14:Supervisor timer
```

Find Sum with Recursion

```
.globl _start
_start:
    li sp, 0x20000
    la s0, N
    lw a0, 0(s0)
    li a1, 0
    jal ra, findsum
    add a1, a1, a0
    return:
        lw a0, 0(sp); lw ra, 4(sp)
        addi sp, sp, 8
    ret
end: j end
findsum: .data
    addi sp, sp, -8 N: .word 5
    sw a0, 0(sp); sw ra, 4(sp)
```